

0-59 up-counter

Rahul Manna

001910501060

BCSE-II

Hardware Design Lab.

Design a counter which counts from 0-59 (up-counter)

For a 0-59 up-counter, we can cascade a decade counter and a Mod 6 counter.

For the decade counter:

Excitation table:

$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$J_3$	$K_3$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	0	0	1	0	x	0	x	0	x	1	x
0	0	0	1	0	0	1	0	0	x	0	x	x	x	x	1
0	0	1	0	0	0	1	1	0	x	0	x	x	0	1	x
0	0	1	1	0	1	0	0	0	x	1	x	x	1	x	1
0	1	0	0	0	1	0	1	0	x	x	0	0	x	1	x
0	1	0	1	0	1	1	0	0	x	x	0	1	x	x	1
0	1	1	0	0	1	1	1	0	x	x	0	x	0	1	x
0	1	1	1	x	0	0	0	1	x	x	1	x	1	x	1
1	0	0	0	1	0	0	1	x	0	0	x	0	x	1	x
1	0	0	1	0	0	0	0	x	1	0	x	0	x	x	1

Minimization:

$J_0$ :

$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00		1	x	x	x
01		1	x	x	1
11		x	x	x	x
10		1	x	x	x

$$J_0 = 1$$

$K_0$ :

$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00		x	1	1	x
01		x	1	1	x
11		x	x	x	x
10		x	1	x	x

$$K_0 = 1$$

J<sub>1</sub> :

$Q_3 Q_2$		$Q_1 Q_0$			
		00	01	11	10
00	0	1	x	x	
01	0	1	x	x	
11	x	x	x	x	
10	0	0	x	x	

$$J_1 = Q_0 \overline{Q_3}$$

K<sub>1</sub> :

$Q_3 Q_2$		$Q_1 Q_0$			
		00	01	11	10
00	x	x	1	0	
01	x	x	1	0	
11	x	x	x	x	
10	x	x	x	x	

$$K_1 = Q_0$$

J<sub>2</sub> :

$Q_3 Q_2$		$Q_1 Q_0$			
		00	01	11	10
00	0	0	1	0	
01	x	x	x	x	
11	x	x	x	x	
10	0	0	x	x	

$$J_2 = Q_1 Q_0$$

K<sub>2</sub> :

$Q_3 Q_2$		$Q_1 Q_0$			
		00	01	11	10
00	x	x	x	x	
01	0	0	1	0	
11	x	x	x	x	
10	x	x	x	x	

$$K_2 = Q_1 Q_0$$

J<sub>3</sub> :

$Q_3 Q_2$		$Q_1 Q_0$			
		00	01	11	10
00	0	0	0	0	
01	0	0	1	0	
11	x	x	x	x	
10	x	x	x	x	

$$J_3 = Q_0 Q_1 Q_2$$

K<sub>3</sub> :

$Q_3 Q_2$		$Q_1 Q_0$			
		00	01	11	10
00	x	x	x	x	
01	x	x	x	x	
11	x	x	x	x	
10	0	1	x	x	

$$K_3 = Q_0$$



For the Mod 6 counter:

Excitation table:

$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	0	0	0	x	1	0	x	x	1

Minimization:

$J_2$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0			0	0	1	0
1			x	x	x	x

$$J_2 = Q_0 Q_1$$

$K_2$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0			x	x	x	x
1			0	1	x	x

$$K_2 = Q_0$$

$J_1$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0			0	1	x	x
1			0	0	x	x

$$J_1 = Q_0 \bar{Q}_2$$

$K_1$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0			x	x	1	0
1			x	x	x	x

$$K_1 = Q_0$$

$J_0$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0			1	x	x	1
1			1	x	x	x

$$J_0 = 1$$

$K_0$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0			x	1	1	x
1			x	1	x	x


$$K_0 = 1$$

### Cascading Logic:

All flipflops are falling edge triggered. Now, the counter only upcounts, so the 10's place changes when the counter on 1's place changes state, from  $(1001)_2$  to  $(0000)_2$ .


$\therefore$  the clock input in the Mod 6 counter in 10's place is high only when the decade counter at 1's place is at state  $(1001)_2$ .


# Mod10 up counter

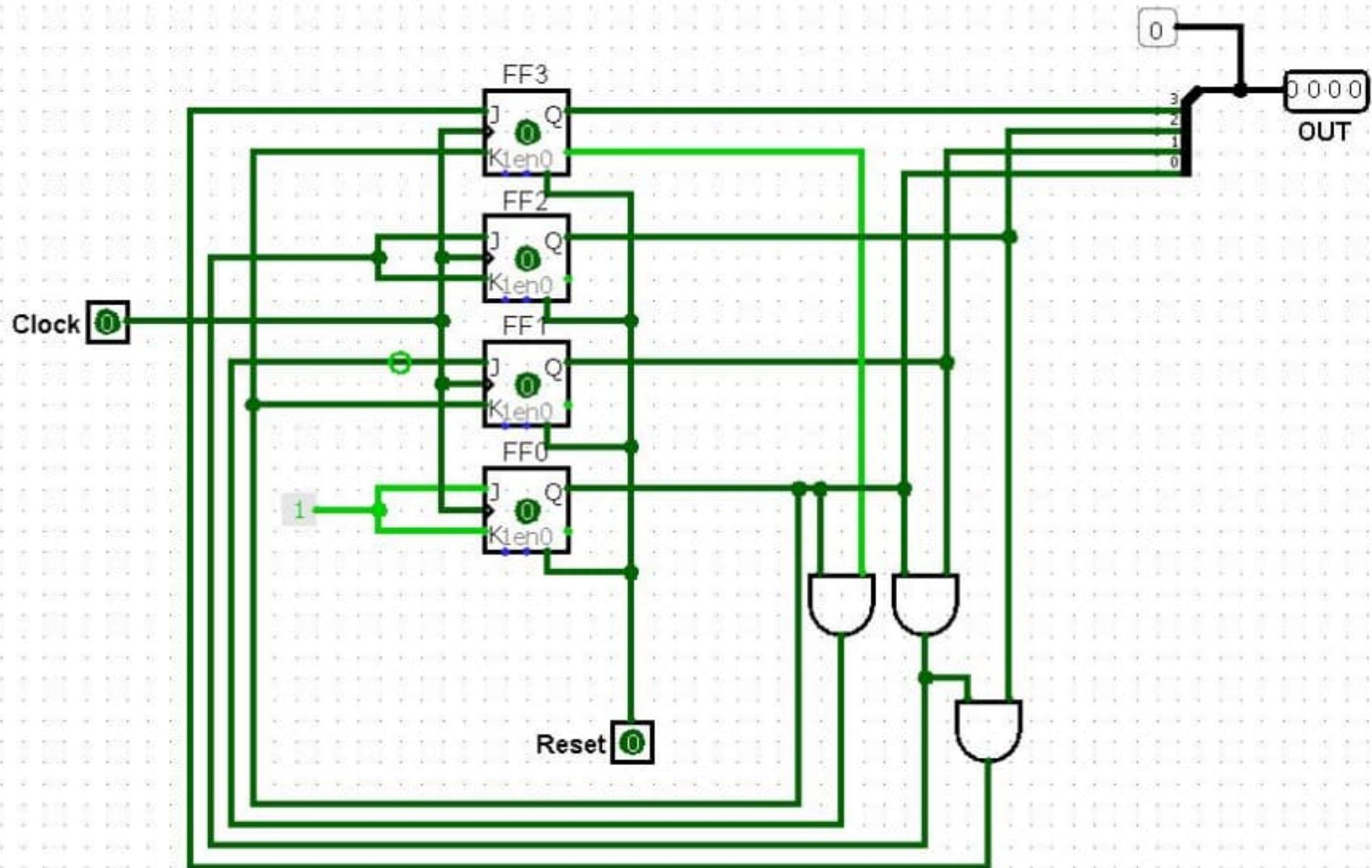



# Mod6 up counter

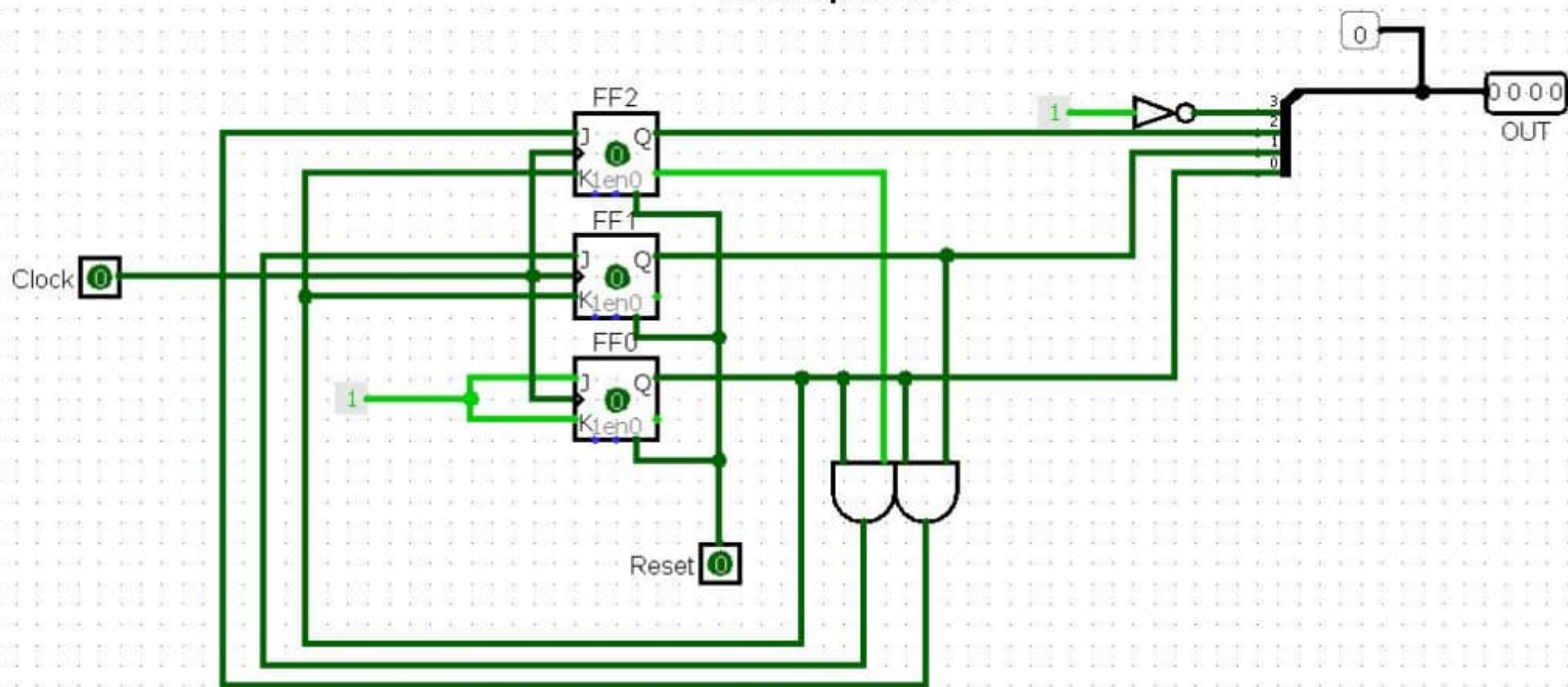

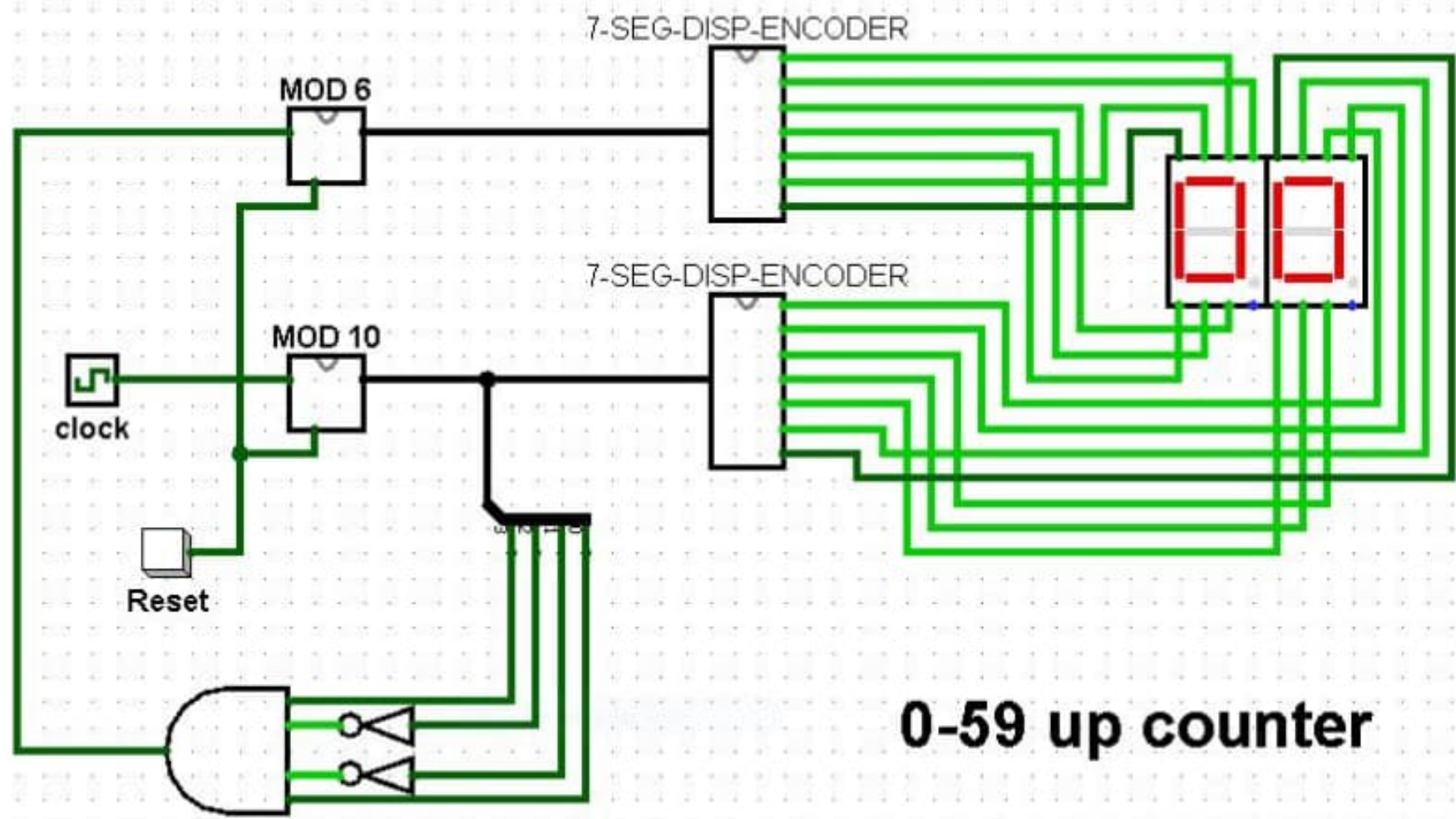

**0-59 up counter**