

Seven Segment Display Encoder

Rahul Manna 001910501066


BCSE-II

Hardware Design Lab.

Design a System to Display 0-9 through a 7-Segment L.E.D. Display.

- A 7-segment LED display has 7 outputs or LEDs, which make combinations to display numbers from 0-9.

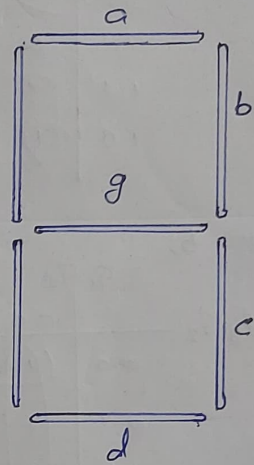Let the LEDs be numbered from 'a' to 'g' as in the Figure. Now, the encoder circuit will have 4 inputs for the decimal number's binary representation and 7 outputs, each corresponding to one of the LEDs.



Truth Table:

Input				Output.						
Q_3	Q_2	Q_1	Q_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

Minimization:

For a,

		q_1, q_0			
$q_3 q_2$		00	01	11	10
	00	1	0	1	1
	01	0	1	1	1
	11	x	x	x	x
	10	1	1	x	x

$$a = \overline{q_2} \overline{q_0} + q_1 + q_3 + q_2 q_0$$

For b,

		q_1, q_0			
$q_3 q_2$		00	01	11	10
	00	1	1	1	1
	01	1	0	1	0
	11	x	x	x	x
	10	1	1	x	x

$$b = \overline{q_2} + \overline{q_1} \overline{q_0} + q_1 q_0$$

For c,

		q_1, q_0			
$q_3 q_2$		00	01	11	10
	00	1	1	1	0
	01	1	1	1	1
	11	x	x	x	x
	10	1	1	x	x

$$c = \overline{q_1} + q_0 + q_2$$

For d,

		q_1, q_0			
$q_3 q_2$		00	01	11	10
	00	1	0	1	1
	01	0	1	0	1
	11	x	x	x	x
	10	1	1	x	x

$$d = \overline{q_2} \overline{q_0} + \overline{q_2} q_1 + q_1 \overline{q_0} + q_2 \overline{q_1} q_0 + q_3$$

For e,

		q_1, q_0			
$q_3 q_2$		00	01	11	10
	00	1	0	0	1
	01	0	0	0	1
	11	x	x	x	x
	10	1	0	x	x

$$e = \overline{q_2} \overline{q_0} + q_1 \overline{q_0}$$

For f ,

		Q_1, Q_0			
Q_3, Q_2		00	01	11	10
	00	1	0	0	0
	01	1	1	0	1
	11	x	x	x	x
	10	1	1	x	x

$$f = Q_3 + Q_2 \bar{Q}_0 + Q_2 \bar{Q}_1 + \bar{Q}_1 \bar{Q}_0$$

For g ,

		Q_1, Q_0			
Q_3, Q_2		00	01	11	10
	00	0	0	1	1
	01	1	1	0	1
	11	x	x	x	x
	10	1	1	x	x

$$g = Q_3 + Q_2 \bar{Q}_0 + Q_2 \bar{Q}_1 + \bar{Q}_2 Q_1$$

Expressions:

$$a = Q_3 + Q_1 + \bar{Q}_2 \bar{Q}_0 + Q_2 Q_0$$

$$b = \bar{Q}_2 + \bar{Q}_1 \bar{Q}_0 + Q_1 Q_0$$

$$c = \bar{Q}_1 + Q_0 + Q_2$$

$$d = Q_3 + \bar{Q}_2 \bar{Q}_0 + \bar{Q}_2 Q_1 + Q_1 \bar{Q}_0 + Q_2 \bar{Q}_1 Q_0$$

$$e = \bar{Q}_2 \bar{Q}_0 + Q_1 \bar{Q}_0$$

$$f = Q_3 + Q_2 \bar{Q}_0 + Q_2 \bar{Q}_1 + \bar{Q}_1 \bar{Q}_0$$

$$g = Q_3 + Q_2 \bar{Q}_0 + Q_2 \bar{Q}_1 + \bar{Q}_2 Q_1$$

