

Up-Down Decade Counter using JK-FlipFlops

Rahul Manna 001910501060

BCSE-II

Hardware Design Lab.


Design an up and down (as selected by a control line) decade counter using JK-FlipFlop.

- the up-down decade counter has 10 states.
If n flipflops are needed, then $2^n \geq 10$.

$\therefore n = 4$, i.e. 4 JK FlipFlops are needed.

Now, when the input/control signal is 0, the counter counts up, and when input is 1, the counter counts down.

State Diagram:

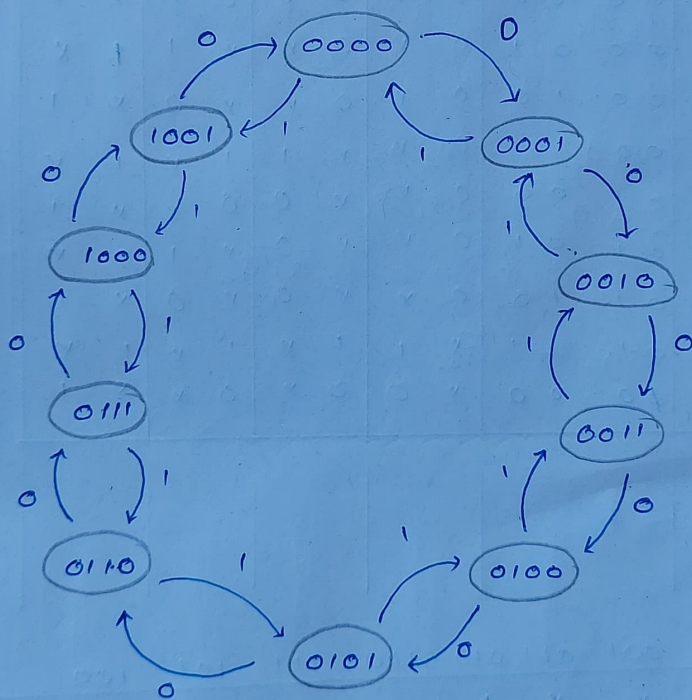

4 flipflops can handle $2^4 = 16$ states.

So there will be 6 invalid states in the state table.

Excitation Table:

control	DS	NS	Flip - flops			
C	$Q_3 Q_2 Q_1 Q_0$	$Q_3^+ Q_2^+ Q_1^+ Q_0^+$	$J_3 K_3$	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$
0	0 0 0 0	0 0 0 1	0 x	0 x	0 x	1 x
0	0 0 0 1	0 0 1 0	0 x	0 x	1 x	x 1
0	0 0 1 0	0 0 1 1	0 x	0 x	x 0	1 x
0	0 0 1 1	0 1 0 0	0 x	1 x	x 1	x 1
0	0 1 0 0	0 1 0 1	0 x	x 0	0 x	1 x
0	0 1 0 1	0 1 1 0	0 x	x 0	1 x	x 1
0	0 1 1 0	0 1 1 1	0 x	x 0	x 0	1 x
0	0 1 1 1	1 0 0 0	1 x	x 1	x 1	x 1
0	1 0 0 0	1 0 0 1	x 0	0 x	0 x	1 x
0	1 0 0 1	0 0 0 0	x 1	0 x	0 x	x 1
1	0 0 0 0	1 0 0 1	1 x	0 x	0 x	1 x
1	0 0 0 1	0 0 0 0	0 x	0 x	0 x	x 1
1	0 0 1 0	0 0 0 1	0 x	0 x	x 1	x 1
1	0 0 1 1	0 0 1 0	0 x	0 x	x 0	x 1
1	0 1 0 0	0 0 1 1	0 x	x 1	1 x	1 x
1	0 1 0 1	0 1 0 0	0 x	x 0	0 x	x 1
1	0 1 1 0	0 1 0 1	0 x	x 0	x 1	1 x
1	0 1 1 1	0 1 1 0	0 x	x 0	x 0	x 1
1	1 0 0 0	0 1 1 1	x 1	1 x	1 x	1 x
1	1 0 0 1	0 0 0 0	x 0	0 x	0 x	x 1

Minimization:

For J_0 :

$Q_3 Q_2$	000	001	011	010	110	111	101	100
00	1	x	x	x	1	x	x	1
01	1	x	x	x	x	x	x	x
11	1	x	x	x	x	x	x	x
10	1	x	x	1	1	x	x	1

$$J_0 = 1$$

For K_0 :

$Q_3 Q_2$	000	001	011	010	110	101	101	100
00	x	1	1	x	x	1	1	x
01	x	1	x	x	x	x	x	x
11	x	1	x	x	x	x	x	x
10	x	1	1	x	x	1	1	x

$$K_0 = 1$$

For J_1

$\Phi_2 \Phi_1 \Phi_0$	000	001	011	010	110	111	101	100
Φ_3	00	0	1	x	x	x	1	0
	01	0	0	x	x	x	x	x
	11	1	0	x	x	x	x	x
	10	0	0	x	x	x	0	1

$$J_1 = \bar{c}\bar{\Phi}_3\Phi_0 + c\Phi_2\bar{\Phi}_0 + c\Phi_3\bar{\Phi}_0$$

For K_1

$\Phi_2 \Phi_1 \Phi_0$	000	001	011	010	110	111	101	100
Φ_3	00	x	x	1	0	0	1	x
	01	x	x	x	x	x	x	x
	11	x	x	x	x	x	x	x
	10	x	x	0	1	0	x	x

$$K_1 = \bar{c}\Phi_0 + c\bar{\Phi}_0$$

For J_2

$\Phi_2 \Phi_1 \Phi_0$	000	001	011	010	110	111	101	100
Φ_3	00	0	0	1	0	x	x	x
	01	0	0	x	x	x	x	x
	11	1	0	x	x	x	x	x
	10	0	0	0	0	x	x	x

$$J_2 = \bar{c}\Phi_1\Phi_0 + c\Phi_3\bar{\Phi}_0$$

For K_2

$\Phi_2 \Phi_1 \Phi_0$	000	001	011	010	110	111	101	100
Φ_3	00	x	x	x	x	0	1	0
	01	x	x	x	x	x	x	x
	11	x	x	x	x	x	x	x
	10	x	x	x	x	0	0	0

$$K_2 = \bar{c}\Phi_1\Phi_0 + c\bar{\Phi}_1\bar{\Phi}_0$$

For J_3

$\Phi_2 \Phi_1 \Phi_0$	000	001	011	010	110	111	101	100
Φ_3	00	0	0	0	0	1	0	0
	01	x	x	x	x	x	x	x
	11	x	x	x	x	x	x	x
	10	1	0	0	0	0	0	0

$$J_3 = \bar{c}\Phi_2\Phi_1\Phi_0 + c\bar{\Phi}_2\bar{\Phi}_1\bar{\Phi}_0$$

For K_3

$Q_2 Q_1 Q_0$	000	001	011	010	110	111	101	100
$\neg Q_3$								
00	x	x	x	x	x	x	x	x
01	0	1	x	x	x	x	x	x
11	1	0	x	x	x	x	x	x
10	x	x	x	x	x	x	x	x

$$K_3 = \neg Q_0 + \neg \bar{Q}_0$$

Expressions:

$$J_0 = 1$$

$$K_0 = 1$$

$$J_1 = \neg \bar{Q}_3 Q_0 + \neg Q_2 \bar{Q}_0 + \neg Q_3 \bar{Q}_0$$


$$K_1 = \neg Q_0 + \neg \bar{Q}_0$$

$$J_2 = \neg Q_1 Q_0 + \neg Q_3 \bar{Q}_0$$

$$K_2 = \neg Q_1 Q_0 + \neg \bar{Q}_1 \bar{Q}_0$$

$$J_3 = \neg Q_2 Q_1 Q_0 + \neg \bar{Q}_2 \bar{Q}_1 \bar{Q}_0$$

$$K_3 = \neg Q_0 + \neg \bar{Q}_0$$

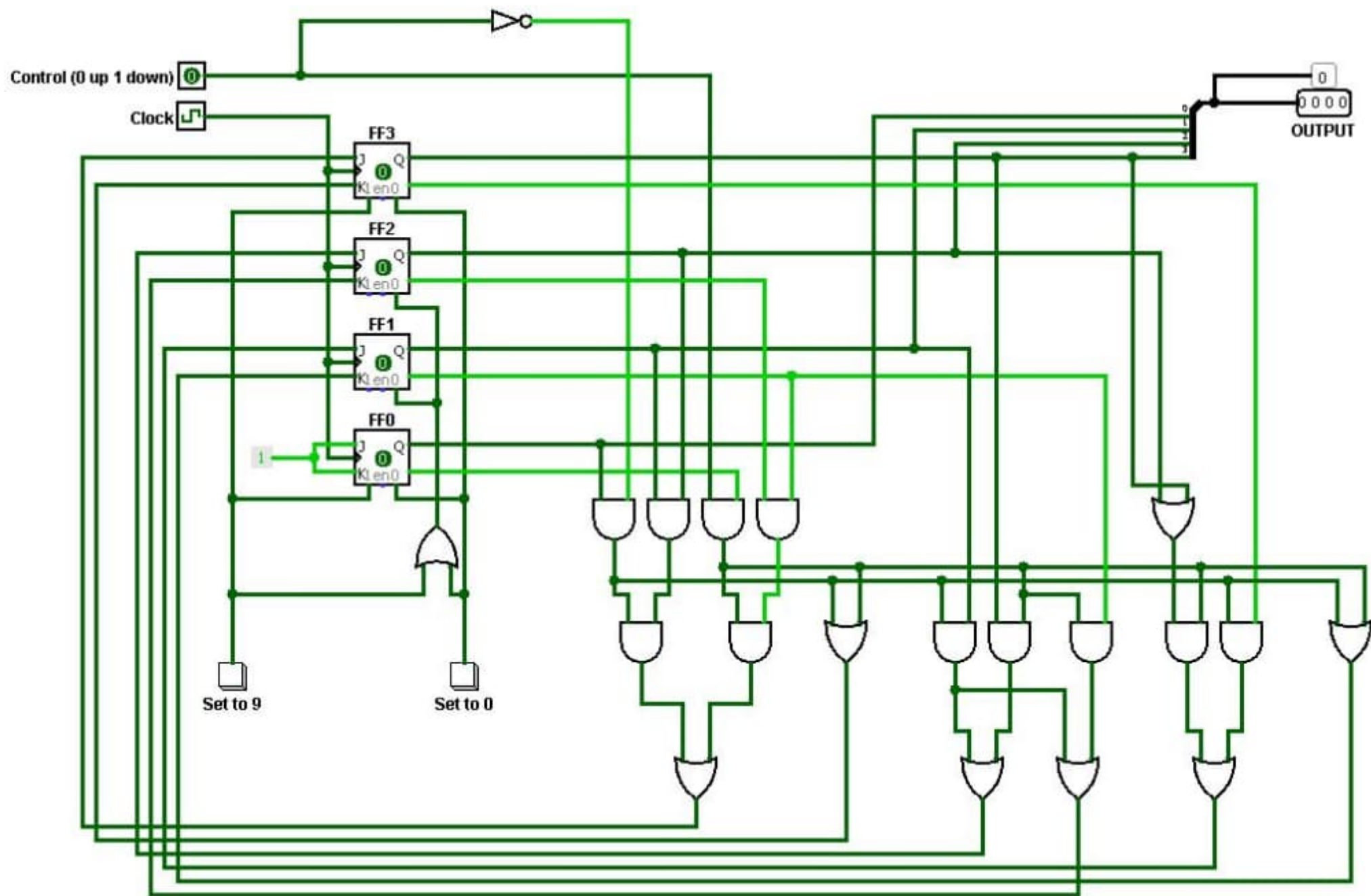

Up-Down Decade Counter Using JK FlipFlops