

4-way Traffic Signal

Rahul Manna

001910501060

TBCSE-II

Hardware Design Lab.



Design a system for a traffic signal at a 4-way crossing.

The 24 hr. clock designed in the previous assignment is used here.

Basic design:

There are 4 lanes. When one lane is open, all others are closed. In this way, when a lane is open, the vehicles can go straight, turn left or turn right without any problem.

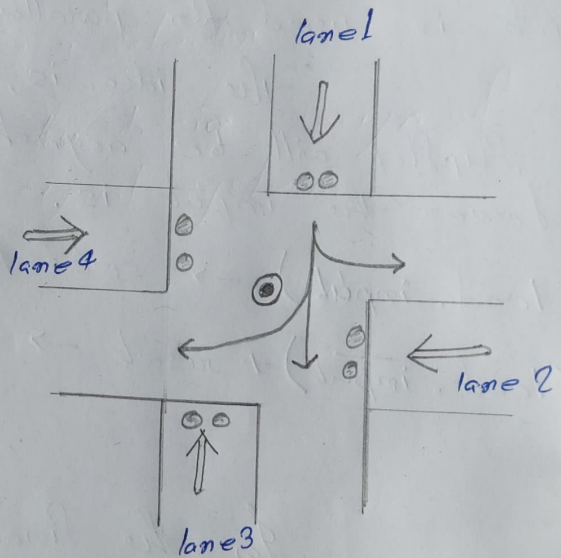


Figure - lane 1 is open

light control:

At every lane, the green light is connected to the control line for that lane, and the red light is complement of the green light line. The control line of a lane is only high, when all other control lines are low. That means, when one lane has a green signal on, all other lanes will have a red signal on.

The control lines are controlled by a mod 4 counter, so that after a certain time interval, the 4 control lines change state.

The time interval between the state change is monitored by a timer. The timer








the mod 4 counter is controlling the 4 way signal switching system.


the 60/30 second timer is controlling the mod 4 counter

the busy hour selector circuit is controlling the timer circuit.

the four outputs of the clock control the busy hour selector

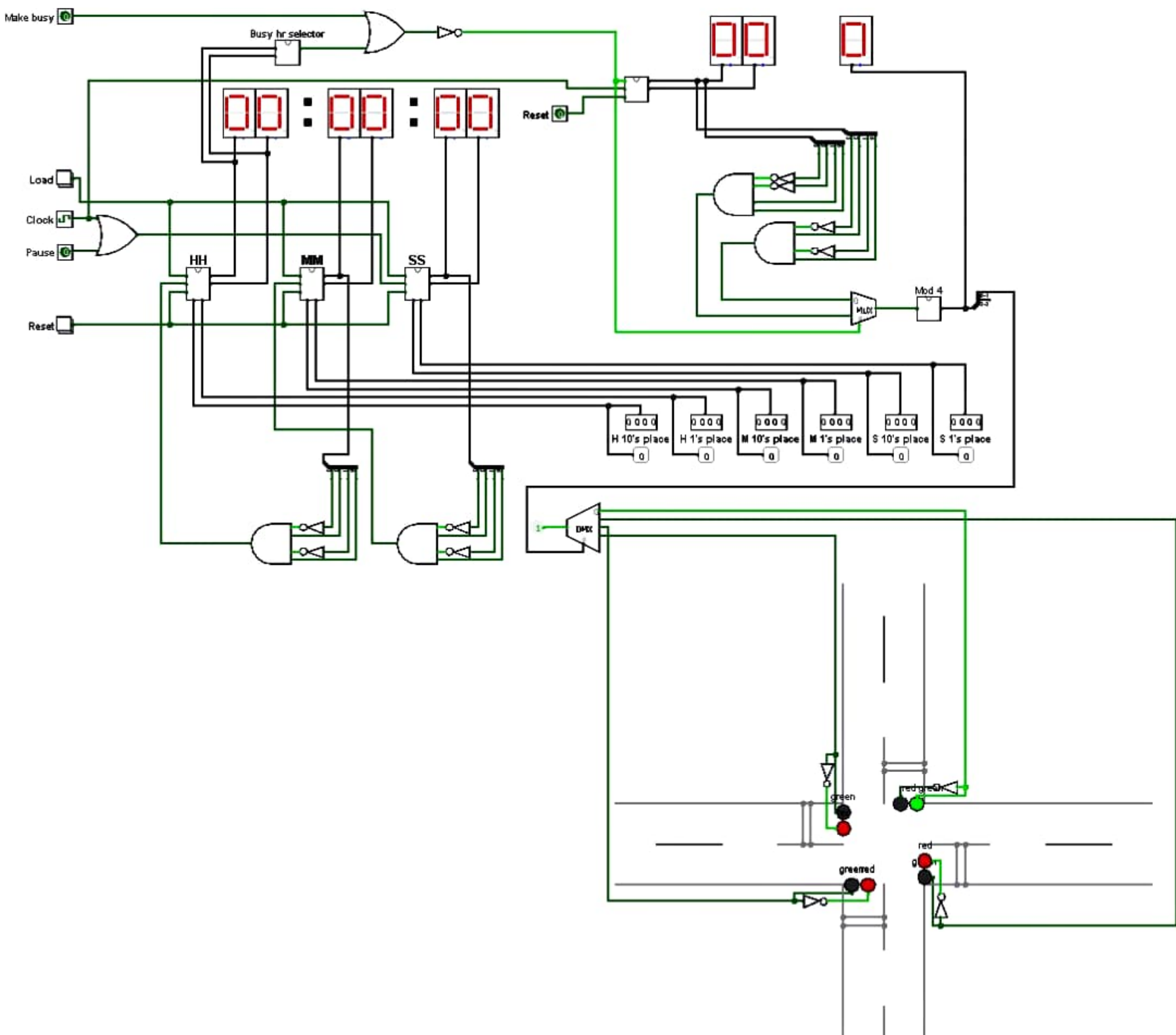— this is the basic design of the 4-way traffic signal system.



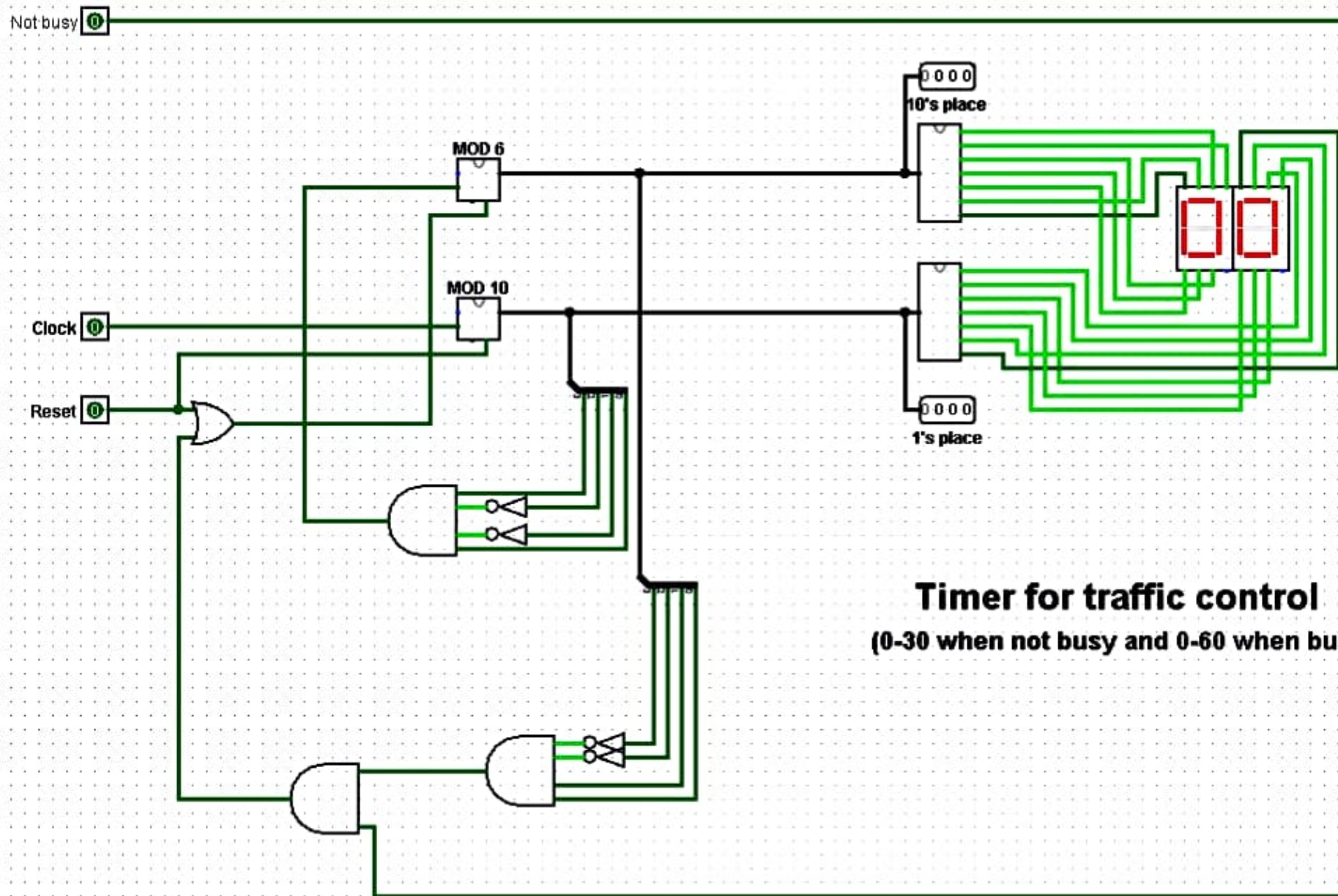

**Timer for traffic control**  
(0-30 when not busy and 0-60 when busy)



## Busy hour selector

**Busy hours : 08:00:00 - 09:59:59 and 17:00:00 - 18:59:59**

